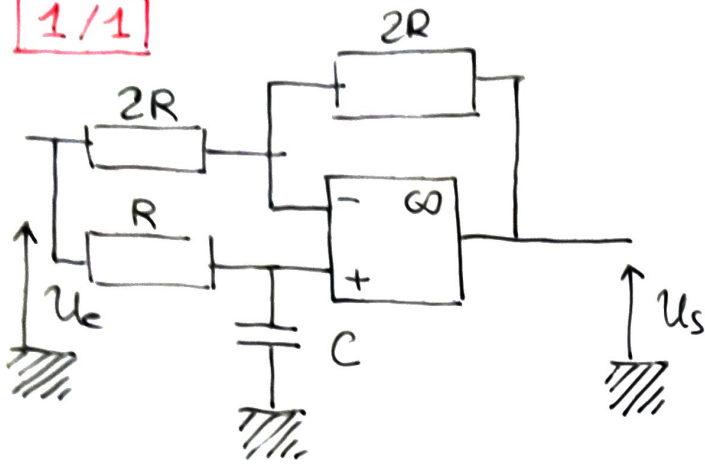


1/1



$$V_- = V_+ \Leftrightarrow \frac{\frac{U_s}{2R} + \frac{U_e}{2R}}{\frac{1}{2R} + \frac{1}{2R}} = \frac{\frac{0}{j\omega C} + \frac{U_e}{R}}{j\omega C + \frac{1}{R}}$$

$$\Leftrightarrow \frac{U_s + U_e}{2} = \frac{U_e}{jx + 1}$$

$$\Leftrightarrow U_s = U_e \left(\frac{2}{jx + 1} - 1 \right)$$

$$\Leftrightarrow \frac{U_s}{U_e} = \underline{H} = \frac{1 - jx}{1 + jx}$$

1/2

$$20 \log |H| = 20 \cdot \log \frac{\sqrt{x^2 + (-1)^2}}{\sqrt{x^2 + 1^2}}$$

$$= 20 \log 1$$


$$= 0 \text{ dB}$$

Posons $\psi := \arg(1 + jx)$ et $\varphi = \arg \underline{H}$

$$\varphi = \arg(1 - jx) - \psi = -\psi - \psi = -2\psi$$


$$\begin{aligned}
 &= -\varphi + \arg(1 + jx) \\
 &= -\varphi - \varphi \\
 &= -2\varphi \\
 &= -2 \arctan x
 \end{aligned}$$

1/3

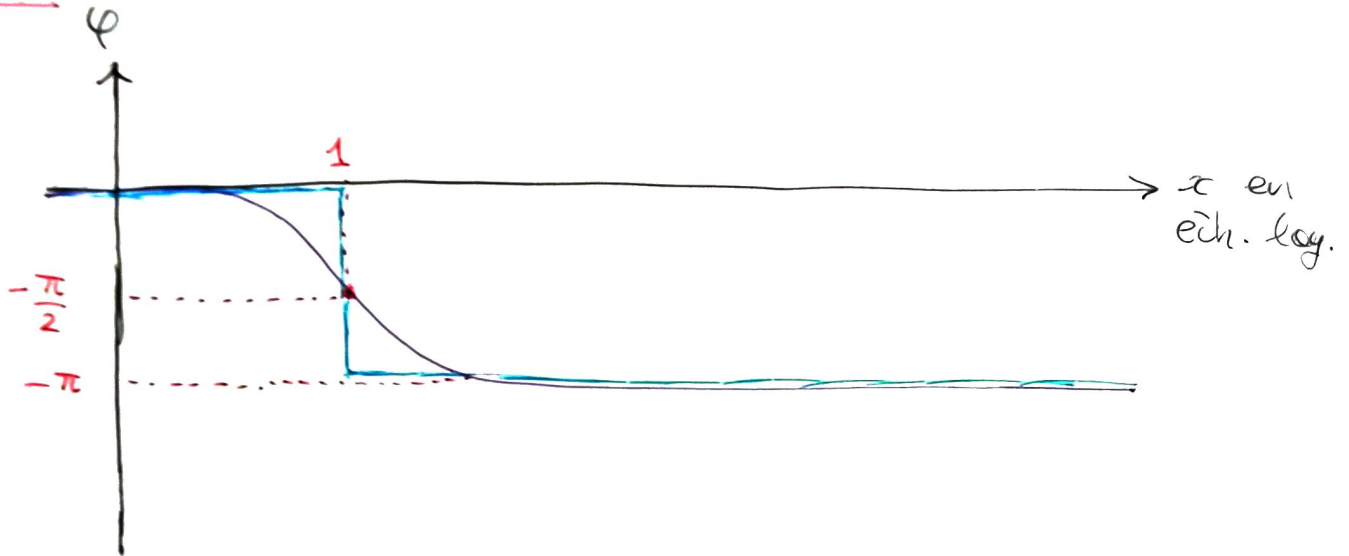


1/4

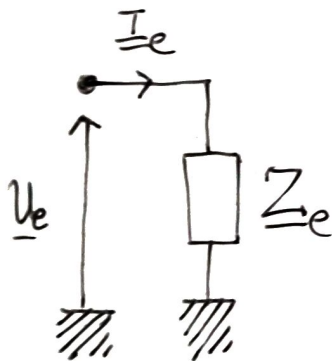Vu de l'entrée, le montage est équivalent à


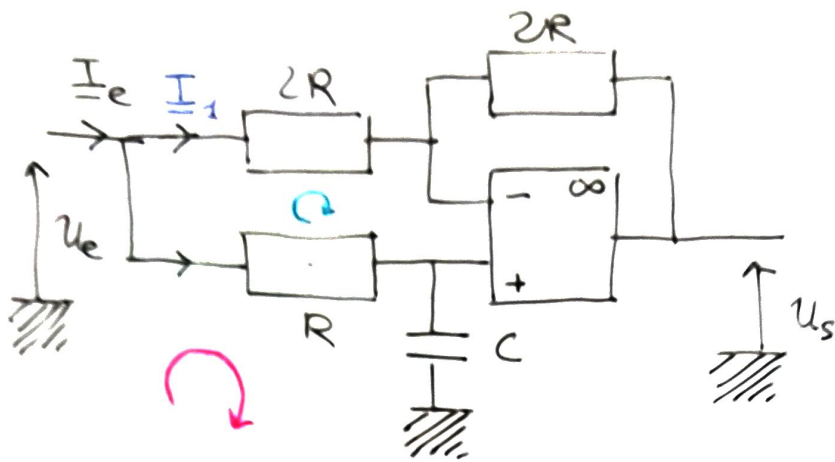
$$\underline{U}_e = \underline{Z}_e \underline{I}_e$$



Maille \odot

$$2R I_1 + R(I_e - I_1) = 0$$

$$\Leftrightarrow -2R I_1 = R(I_e - I_1)$$

$$\Leftrightarrow I_e = 3I_1$$


Maille \ominus

$$u_e - \left(R + \frac{1}{j\omega C}\right)(I_e - I_1) = 0$$

$$u_e = \left(R + \frac{1}{j\omega C}\right) \left(\frac{2}{3} I_e\right)$$

$$= \underbrace{\frac{2}{3} \left(R + \frac{1}{j\omega C}\right)}_{Z_e} I_e$$

3/1

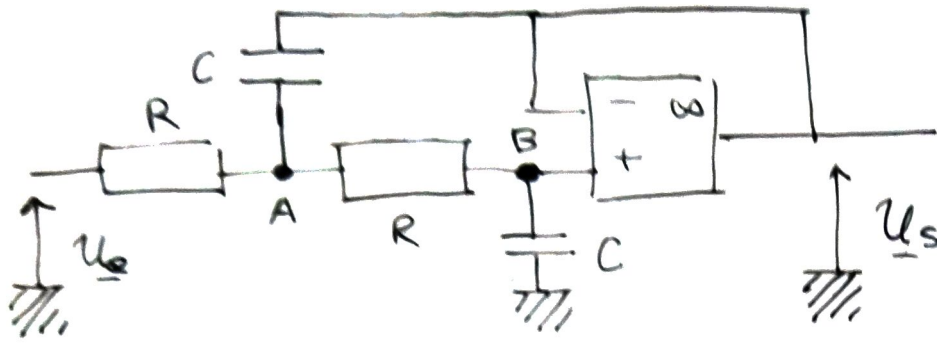

$$V_+ = V_B = \frac{0j\omega C + \frac{V_A}{R}}{j\omega C + \frac{1}{R}} = V_- = \frac{V_A}{jRC\omega + 1} = \underline{u_s}$$

$$V_A = \frac{\frac{u_e}{R} + \frac{V_B}{R} + j\omega C u_s}{\frac{1}{R} + \frac{1}{R} + j\omega C}$$

$$= \frac{u_e + V_B + jRC\omega u_s}{2 + jRC\omega}$$

$$= \frac{u_e + u_s + jRC\omega u_s}{2 + jRC\omega}$$

$$= \frac{u_e + u_s(1 + jRC\omega)}{2 + jRC\omega}$$


$$(1 + jRC\omega)u_s = \frac{u_e + u_s(1 + jRC\omega)}{2 + jRC\omega}$$

$$u_s((1 + jRC\omega)(2 + jRC\omega) - (1 + jRC\omega)) = u_e$$

$$\Leftrightarrow \underline{H} = \frac{1}{(1 + jRC\omega)(2 + jRC\omega) - (1 + jRC\omega)} = \frac{1}{(1 + jx)^2}$$

3/2

$$|H| = \frac{1}{\sqrt{1^2 + x^2}} = \frac{1}{1 + x^2} = G$$

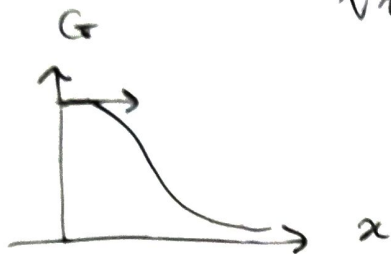

≈ passe-bas

On veut

$$G(x_c) = \frac{\max G}{\sqrt{2}}$$

$$\Leftrightarrow G(x_c) = \frac{1}{\sqrt{2}}$$

$$\Leftrightarrow \frac{1}{1 + x_c^2} = \frac{1}{\sqrt{2}}$$

$$\Leftrightarrow 1 + x_c^2 = \sqrt{2}$$

$$\Leftrightarrow x_c = \sqrt{\sqrt{2} - 1}$$

3/4

